



Code No. : 6086/S

FACULTY OF ENGINEERING
B.E. 3/4 (EEE) I Semester (Supple.) Examination, July 2014
POWER SYSTEMS – II

Time : 3 Hours]

[Max. Marks : 75

Note : Answer **all** questions from Part – **A** and **any five** questions from Part – **B**.

PART – A

1. For a medium length nominal π transmission line draw the circuit and the phasor diagram for lagging power factor conditions. 2
2. Obtain the exact condition for zero regulation for a short transmission lines. 3
3. Show that the load voltage V_2 is not affected much due to the component of the load. 3
4. Compare series and shunt capacitor for voltage control. 2
5. List out the advantages of p.u. systems. 2
6. A transformer is rated at 11 kV/0.4 kV, 500 kVA, 5.2% reactance. Determine the short circuit MVA of the transformer when it is connected to an infinite bus. 3
7. Draw the connection of sequence networks for Double line to ground fault through an impedance Z_r . 2
8. Derive the expression for fault current for a single line to ground fault of an unloaded alternator. 3
9. Draw the travelling waves on a line terminated by inductance and capacitance. 3
10. Explain why a travelling wave suffers reflection when it reaches a discontinuity? 2


PART – B

11. A 3 phase transmission line, 165 km long, transmits a load of 95,000 kW at 0.80 p.f. lagging. The line voltage at the receiving end is 230 kV. The constants of the line are as follows :
 $A = D = 0.9785 \angle 0.3^\circ$ $B = 85.2 \angle 77.47^\circ$ and $C = 0.000503 \angle 90.1^\circ$
Construct the receiving end and sending end circle diagrams for the transmission line and calculate :
 - a) Sending end voltage, current, power factor, regulation and efficiency of the transmission line.
 - b) The load in kW at 0.08 p.f lagging that could be carried at 8% regulation. 10


(This paper contains 3 pages)



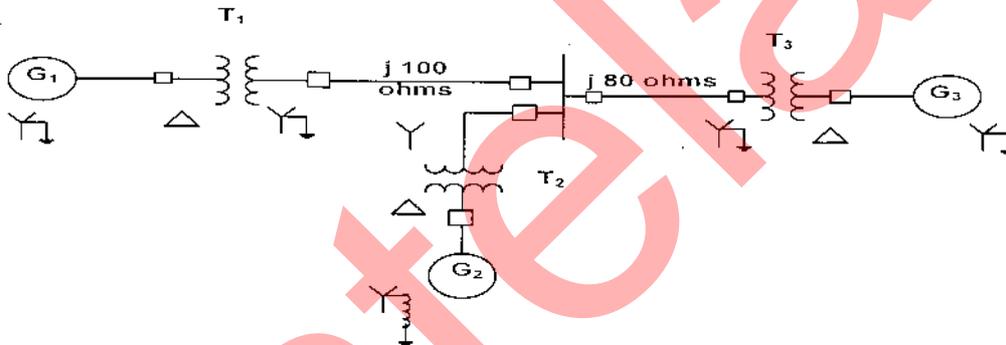12. a) Explain the method of capacity of synchronous phase modifier capacity using graphical method. 6
b) Explain the principle of operation of thyristor switched capacitors. 4
13. The single line diagram of an unloaded power system is shown in below fig. The generator and transformers are rated as follows :
 $G_1 = 20 \text{ MVA}, 13.8 \text{ kV}, X'' = 20\%$, $G_2 = 30 \text{ MVA}, 18 \text{ kV}, X'' = 20\%$,
 $G_3 = 30 \text{ MVA}, 20 \text{ kV}, X'' = 20\%$, $T_1 = 25 \text{ MVA}, 220/13.8 \text{ kV}, X = 10\%$,
 $T_2 = 3 \text{ single phase units each rated at } 10 \text{ MVA}, 127/18 \text{ kV}, X = 10\%$,
 $T_3 = 30 \text{ MVA}, 220/22 \text{ kV}, X = 10\%$. Draw the reactance diagram using a base value of 50MVA and 13.8 kV on the generator G_1 . 10



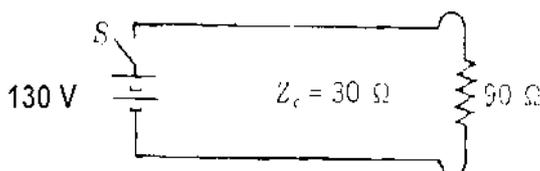14. A salient pole generator without dampers is rated 20 MVA, 13.8 kV and has a direct axis subtransient reactance of 0.25 p.u. The negative and zero sequence reactance are 0.35 and 0.10 p.u. respectively. The neutral of the generator is solidly grounded. Determine the sub-transient current in the generator and the line-to-line voltages for subtransient conditions when a single line-to-ground fault occurs at the generator terminals with generator operating unloaded at rated voltage. Neglect resistance. 10
15. a) A dc source of 110 V with negligible resistance is connected through switch S to a lossless transmission line having $Z_c = 30 \text{ ohms}$. The line is terminated in a resistance of 90 ohms. If the switch closes at $t = 0$, plot v_R versus time until $t = 5T$, where T is the time for a voltage wave to travel through the length of the line. 6



- b) Obtain the transmission line coefficient for voltage and current for a line terminating with two dissimilar lines. 4