

FACULTY OF ENGINEERING

B.E. 2/4 (E&EE.) II – Semester (Main) Examination, April / May 2013

Subject : Electrical Circuits – II

Time : 3 hours

Max. Marks : 75

Note: Answer all questions from Part-A. Answer any FIVE questions from Part-B.

PART – A (25 Marks)


1. A series RL circuit is excited by a unit step excitation. Then find the circuit response $i(t)$ in the circuit. (3)
2. Define final value theorem. (3)
3. Mention any three necessary conditions that must be satisfied by driving point admittance functions. (3)
4. Find $f(0)$ and $f(\infty)$ for the below function. (4)

$$F(s) = \frac{s + 4}{s(s + 1)(s + 5)}$$


5. Define 'odd function symmetry'. (3)
6. Find the Fourier transform of $f(t) = e^{j\omega_0 t}$ (2)
7. Determine whether the function $F(s) = s^6 + 5s^5 + 12s^4 + 16s^3 + 12s^2 + 4s$ is Hurwitz. (3)
8. Synthesize the first Foster term of $z(s) = \frac{(s^2 + 2)(s^2 + 4)}{s(s^3 + 3)}$ (4)

PART – B (50 Marks)

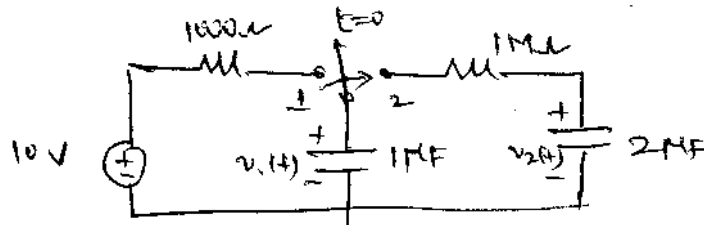
9. Find $v_1(t)$ and $v_2(t)$ for $t > 0$ in the network shown below. The switch was in position 1 for a long time before it is thrown to position 2. (10)



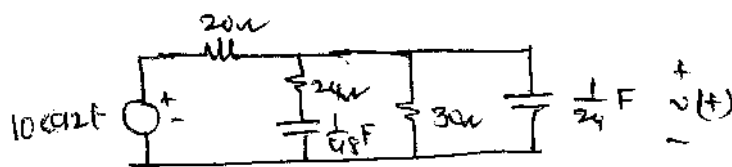
10. Find $v(t)$ for the circuit shown below, using the Laplace transforms method of analysis. (10)



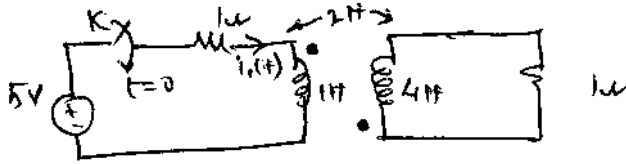11. Find current $i_1(t)$ for $t > 0$ if the switch 'k' is closed at $t = 0$ in the below circuit. (10)



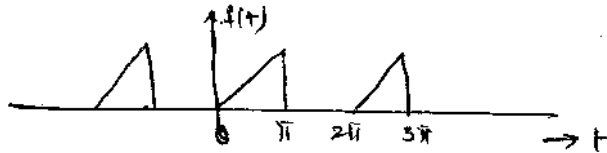12. Find the Fourier series of the waveform show below. Hence find the Fourier series. (10)



13. Synthesize the two carrer forms for the impedance function $z(s) = \frac{(s+3)(s+8)}{(s+2)(s+1)}$ (10)

- 14.a) Write the properties of driving point function $z(s)$ of RC network. (5)

- b) Synthesis the second Foster forms for the impedance function (5)

$$z(s) = \frac{(s+1)(s+4)}{(s+2)}$$

- 15.a) Find the Fourier transforms for the following function. (6)

i) $u_0(t - t_0)$ ii) $ca(2t + 45)$

- b) State and explain complex translation theorem. (4)
