



Code No. : 6125

FACULTY OF ENGINEERING

B.E. 2/4 (ECE) II Semester (Main) Examination, June 2010  
PULSE, DIGITAL AND SWITCHING CIRCUITS

Time: 3 Hours]

[Max. Marks: 75

Note : Answer all questions from Part A. Answer any five questions from Part B.

PART - A

(25 Marks)

1. Show the circuit of a compensating attenuator and give the relation for proper compensation. 3
2. \_\_\_\_\_ multivibrator can be used as a voltage to frequency converter. (Astable/Monostable/Bistable) 2
3. Compare the performance of series clipper with shunt clipper. 2
4. What is the principle of Miller sweep circuits ? 2
5. Prove that NAND gate is an universal gate. 2
6. Show a prime implicant chart and comment on the reduction procedure. 2
7. Discuss the procedure adopted for testing a function for symmetry. 3
8. Design half subtractor with NAND gates only. 3
9. Convert 'D' flip flop to 'T' flip flop. 3
10. Write the truth table of SR, JK, T and D flip flop. 3

PART - B

(50 Marks)

11. a) Why a High Pass RC circuit is called a differentiator ? 3
- b) A symmetrical square wave whose average value is zero has a peak to peak amplitude of 20 volts and a period of 2 micro second. This waveform is applied to a low-pass circuit whose upper 3dB frequency is  $\frac{1}{2} \pi$  MHz. Calculate and sketch the steady state output waveform. In particular, what is the peak-to-peak output amplitude ? 7

12. a) With references the binary circuit, explain the role of the commutating capacitors. 3  
 b) Design an Astable multivibrator to generate a 5 KHz square wave with a duty cycle equal to 60% amplitude 10 volts. Use NPN transistor having  $h_{FE}(\min) = 60$ ,  $I_{C(\max)} = 50$  mA,  $V_{BE(\text{sat})} = 0.7$  volt,  $V_{CE(\text{sat})} = 0.2$  volt. Show the circuit diagram and all the waveforms. 7
13. a) Discuss the various methods of improving sweep linearity in voltage time base generators and derive the expression for sweep speed error in each case. 5  
 b) Draw the circuit diagram of a Boot strap voltage time base generators and explain its operation with waveforms. Derive the expression for its sweep amplitude, sweep period, retrace interval and recovery time. 5
14. a) Using Switching algebra simplify the following expressions :  
 i)  $f(w, x, y, z) = x + xyz + \bar{x}yz + wx + \bar{w}x + \bar{x}y$   
 ii)  $f(w, x, y, z) = (w + x + y + z)(x + y + z)(y + z)(z)$ . 6  
 b) Find the TT for the following switching function :  
 $f(A, B, C, D) = AB\bar{C}D + ABC\bar{D}$ . 4
15. For the function  
 $T(w, x, y, z) = \sum m(0, 1, 2, 3, 4, 6, 7, 8, 9, 11, 15) + \sum d(10, 13)$   
 a) Find all prime implicants. 5  
 b) Find the essential prime implicants. 5
16. Design MOD-13 synchronous counter using T-FF. Explain all design steps clearly. Draw its output with respect to clock input. 10
17. Write short notes on **any two** : (5×2=10)  
 a) UJT  
 b) Clamping theorem  
 c) Contact N.W.