

FACULTY OF ENGINEERING

B.E. 2/4 (ECE) I – Semester (Main) Examination, Nov./Dec. 2012

Subject: Electronic Devices

Time: 3 Hours

Max. Marks: 75

Note: Answer all questions from Part A. Answer any five questions from Part B.**PART – A (25 Marks)**

1. Differentiate between transition capacitance and diffusion capacitance of a P-N junction diode. (2)
2. Determine a.c resistance for semiconductor diode with a forward bias of 0.25 V. Reverse saturation current at room temperature is of $1.2\mu\text{A}$. (3)
3. Why is bleeder resistance employed in a filter circuit? (2)
4. In a bridge rectifier circuit peak value of secondary voltage is $240\sqrt{2}$ V and frequency is 50 Hz. Determine the (i) No load output D.C. voltage (ii) Output frequency. (3)
5. A transistor has $\alpha=0.98$. If emitter current of the transistor is 1 mA, determine base current and gain factor ' β '. (3)
6. What is early effect? Explain how it affects the BJT characteristics in CB configuration. (2)
7. How does a UJT differ from a FET? (3)
8. Draw the equivalent h-parameter model for C.B configuration. (2)
9. What is meant by depletion region in JFET? Explain. (2)
10. Prove that the trans conductance g_m of JFET is given by $g_m = \frac{.2}{|V_p|} \sqrt{I_{DS} \cdot I_{DSS}}$ (3)

PART – B (50 Marks)

11. (a) The reverse bias saturation current for a P-N junction diode is $1\mu\text{A}$ at 300°K . Determine its a.c resistance at 150 mV forward bias. (4)
- (b) Explain the working of P-N junction under forward bias and reverse bias with neat circuit diagrams. (6)
12. (a) Design a filter for full wave rectifier circuit with LC filter to provide an output voltage of 25V with a load current of 100 mA and its ripple is limited to 3%. (6)
- (b) Explain the construction and working principle of LED. What are the merits of LED's. (4)
13. (a) Draw the circuit of self-biased CE-amplifier using diode compensation for I_{CO} . Describe how bias compensation is achieved. (6)
- (b) Distinguish between d.c and a.c load lines with suitable examples. (4)
14. A C.E amplifier is driven by a voltage source of internal resistance $R_s = 800 \Omega$, the load impedance is a of $2 \text{ k}\Omega$. The h-parameters are $h_{ie} = 1.1 \text{ k}\Omega$, $h_{fe} = 50$, $h_{oe} = 25 \text{ Micro ohms}$, $h_{re} = 2.5 \times 10^{-4}$. Compute the current gain A_i , input resistance R_i , voltage gain A_v , output resistance R_o and output terminal resistance R_{o1} . Also calculate power gain A_p using approximate analysis. (10)
15. (a) Explain the construction and working of a TRIAC. Sketch its V-I characteristics. (6)
- (b) Write a short notes on CCD. (4)
16. (a) Explain the basic construction of a n-channel depletion type MOSFET. Draw and explain its characteristics. (6)
- (b) What are the advantages of MOSFET over JFETs? (4)
17. Write a short notes on:
 - (a) Compensation techniques (4)
 - (b) LCD (3)
 - (c) Varactor diode (3)