

## FACULTY OF ENGINEERING

B.E. 2/4 (EE/Inst.) II Semester (Main) Examination, May/June 2011

### ELECTRONIC ENGINEERING-II

Time : 3 Hours ]

[ Max. Marks : 75

**Note :** Answer **all** questions from Part – A. Answer any **five** questions from Part – B.

#### PART – A

(Marks : 25)


1. Explain why the CMRR is infinite if a true current constant source is used in a symmetrical emitter-coupled difference amplifier.
2. How does a voltage series negative feedback alter the input and output impedances of an amplifier ?
3. Draw the equivalent circuit of a crystal and define series and parallel resonances of the crystal.
4. Specify the type of components  $Z_i$ ,  $Z_o$  and  $Z_f$  for a colpitts oscillator and sketch its circuit diagram.
5. What is meant by operation of amplifiers in Class A, Class B and Class C ?
6. A resistive load of  $4 \Omega$  is matched to the collector impedance of an amplifier by means of a transformer having turns ratio of 40 : 1. What is the reflected impedance ?
7. Define rise time and delay time of a low pass filter for a step input.
8. What is meant by linear wave shaping ?
9. A difference amplifier has a CMRR of  $60\text{dB}$  and  $A_d = 1000$ . Find  $A_C$  in dB.
10. In a BJT self bias circuit, which type of negative feedback is used ? Justify.

#### PART – B

(Marks : 50)

11. (a) Derive the equation for  $A_f$ , the gain with feedback, for a negative feedback amplifier.
- (b) Explain clearly how negative feedback effects the amplifier input and output impedances and derive  $R_{if}$  for shunt input connection.

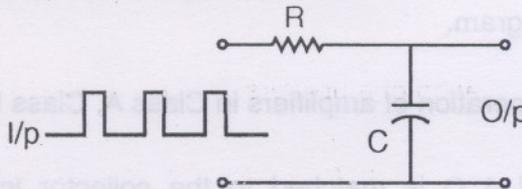12. (a) Derive an expression for frequency of oscillations of an RC phase shift oscillator and justify the Barkhausen conditions in this case.
- (b) Find  $C$  and  $h_{fe}$  of a transistor to provide  $f_o$  of 50 KHZ of a RC transistorized phase shift oscillator. Given  $R_1 = 22 \text{ K}\Omega$ ,  $R_2 = 68 \text{ K}\Omega$ ,  $R_C = 20 \text{ K}\Omega$ ,  $R = 6.8 \text{ K}\Omega$  and  $h_{ie} = 2 \text{ K}\Omega$ .
13. (a) Define  $A_C$ ,  $A_D$  and CMRR of a difference amplifier.
- (b) A difference amplifier has inputs  $V_{S1} = 10 \text{ mV}$ ,  $V_{S2} = 9 \text{ mV}$ . If it has  $A_D = 60 \text{ dB}$  and  $\text{CMRR} = 80 \text{ dB}$ , find the percentage error in the output and the error voltage.
14. (a) Show that the output of a push pull amplifier does not contain even harmonics.
- (b) If an amplifier draws 800 mA from a 10 V d.c. supply and delivers 6 Watts of audio power to a loud speaker, calculate : (i) d.c. power (ii) collector power dissipation (iii) conversion efficiency.
15. (a) Draw the response of the following circuit to the input given. Is it a differentiator or an integrator ? Why ?



- (b) Justify why a clamping circuit is called a d.c. restorer.
- (c) What is a clipper ? Discuss.
16. (a) What is cross over distortion in power amplifiers ?
- (b) What is frequency stability with respect to oscillators ?
17. Write notes on any **two** :
- (a) Drift compensation techniques
- (b) Complementary symmetry amplifier
- (c) Effect of feedback on noise of an amplifier